

## LAB #09

**Objective:** Implementation of Simple RC Circuits and finding its response.

**Exercise#01:** Apply the above code in PSpice and show the output and verify the result with manual calculation.

**Example #01:**

Va 1 0 72V

R1 1 2 2ohm

C1 1 2 2uF

R2 2 0 7ohm

C2 2 3 3uF

R3 3 0 8ohm

.DC Va 0 72 72

.PRINT DC V(R1) V(R2) V(R3) V(C1) V(C2)

.PRINT DC I(R1) I(R2) I(R3) I(C1) I(C2)

.options nopage

.END

**Output:**

\*\*\*\* 04/17/21 08:49:33 \*\*\*\*\* PSpice 9.2 (Mar 2000) \*\*\*\*\* ID# 1 \*\*\*\*\*

Name: Ahmad Baseer Roll no:124

\*\*\*\* CIRCUIT DESCRIPTION

\*\*\*\*\*

Va 1 0 72V

R1 1 2 2 ohm

C1 1 2 2uF

R2 2 0 7 ohm

C2 2 3 3uF

R3 3 0 8 ohm

.DC Va 0 72 72

.PRINT DC V(R1) V(R2) V(R3) V(C1) V(C2)

.PRINT DC I(R1) I(R2) I(R3) I(C1) I(C2)

.options nopage

.END

\*\*\*\* DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

Va	V(R1)	V(R2)	V(R3)	V(C1)	V(C2)
----	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------


7.200E+01	1.600E+01	5.600E+01	0.000E+00	1.600E+01	5.600E+01
-----------	-----------	-----------	-----------	-----------	-----------

\*\*\*\* DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

Va	I(R1)	I(R2)	I(R3)	I(C1)	I(C2)
----	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------

7.200E+01	8.000E+00	8.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------

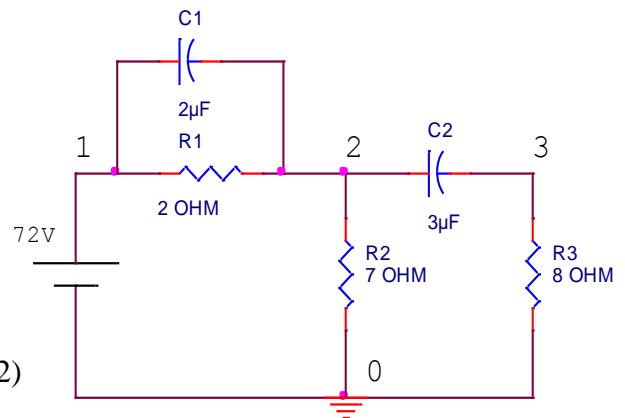


**Exercise#02: Write down the code in PSpice and find the voltage and current across each component (resistors and capacitor) .****Code:**

```

V1 1 0 20V
R1 1 2 124 ohm
C1 1 2 6uF
R2 2 0 124 ohm
C2 2 0 10uF
R3 2 0 124 ohm
.DC V1 0 20 20
.PRINT DC V(R1) V(R2) V(R3) V(C1) V(C2)
.PRINT DC I(R1) I(R2) I(R3) I(C1) I(C2)
.options nopage
.END

```

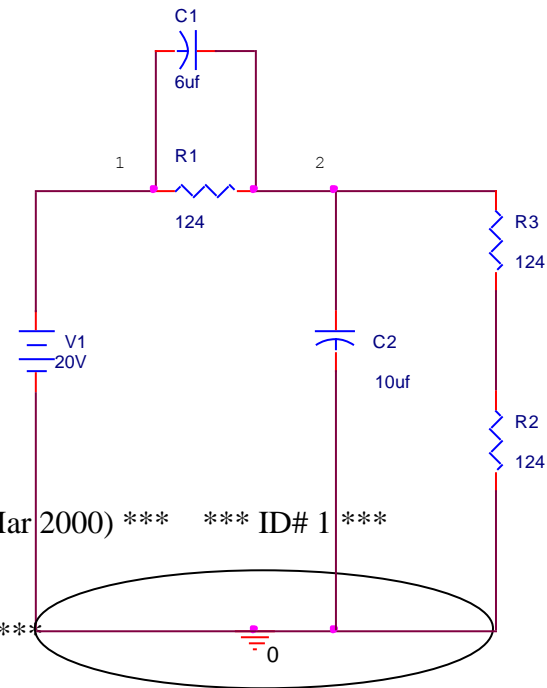**Output:**

```

**** 04/17/21 09:10:00 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer Roll no:124
**** CIRCUIT DESCRIPTION ****
*****
V1 1 0 20
R1 1 2 124
C1 1 2 6uF
R2 2 0 124
C2 2 0 10uF
R3 2 0 124
.DC V1 0 20 20
.PRINT DC V(R1) V(R2) V(R3) V(C1) V(C2)
.PRINT DC I(R1) I(R2) I(R3) I(C1) I(C2)
.options nopage
.END
**** 04/17/21 09:10:00 **** PSpice 9.2(Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer Roll no:124**** DC TRANSFER CURVES
TEMPERATURE = 27.000 DEG C
*****
V1      V(R1)      V(R2)      V(R3)      V(C1)      V(C2)

0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00
2.000E+01 1.333E+01 6.667E+00 6.667E+00 1.333E+01 6.667E+00

**** 04/17/21 09:10:00 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer Roll no:124
**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C ****
*****
V1      I(R1)      I(R2)      I(R3)      I(C1)      I(C2)

0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00
2.000E+01 1.075E-01 5.376E-02 5.376E-02 0.000E+00 0.000E+00


```

**Exercise#03: Write down the code in PSpice and find the voltage and current across each component (resistors and capacitor).****Code:**

```

V1 1 0 1
R1 4 0 2k
C1 3 0 1uF
R2 4 3 4k
R3 3 1 1k
R4 3 0 6k
R5 1 2 5k
R6 2 0 2k
.DC V1 0 1 1
.PRINT DC V(R1) V(R2) V(R3) V(C1) V(R4) V(R5) V(R6)
.PRINT DC I(R1) I(R2) I(R3) I(C1) I(R4) I(R5) I(R6)
.options nopage
.END

```

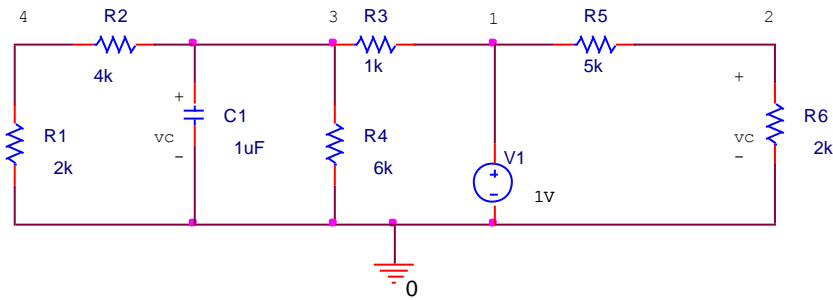**Output:**

\*\*\*\* 04/17/21 09:51:38 \*\*\*\*\* PSpice 9.2 (Mar 2000) \*\*\*\*\* ID# 1 \*\*\*\*\*

Name: Ahmad Baseer Roll no:124

\*\*\*\* CIRCUIT DESCRIPTION

\*\*\*\*\*

```

V1 1 0 1V
R1 4 0 2k ohm
C1 3 0 1uF
R2 4 3 4k ohm
R3 3 1 1k ohm
R4 3 0 6k ohm
R5 1 2 5k ohm
R6 2 0 2k ohm
.DC V1 0 20 20
.PRINT DC V(R1) V(R2) V(R3) V(C1) V(R4) V(R5) V(R6)
.PRINT DC I(R1) I(R2) I(R3) I(C1) I(R4) I(R5) I(R6)
.options nopage
.END

```

```

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C
V1      V(R1)      V(R2)      V(R3)      V(C1)      V(R4)
0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00
1.000E+00 2.500E-01 -5.000E-01 -2.500E-01 7.500E-01 7.500E-01

```

```

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C
V1      V(R5)      V(R6)
0.000E+00 0.000E+00 0.000E+00
1.000E+00 7.143E-01 2.857E-01

```

```

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C
V1      I(R1)      I(R2)      I(R3)      I(C1)      I(R4)
0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00 0.000E+00
1.000E+00 1.250E-04 -1.250E-04 -2.500E-04 0.000E+00 1.250E-04
**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C
V1      I(R5)      I(R6)
0.000E+00 0.000E+00 0.000E+00
1.000E+00 1.429E-04 1.429E-04

```