

LAB #06


Objective: Implementation of Series-Parallel Resistive Network in PSpice.

Exercise #01: Apply the above three codes in PSpice and show the output and verify their result via manual calculation.

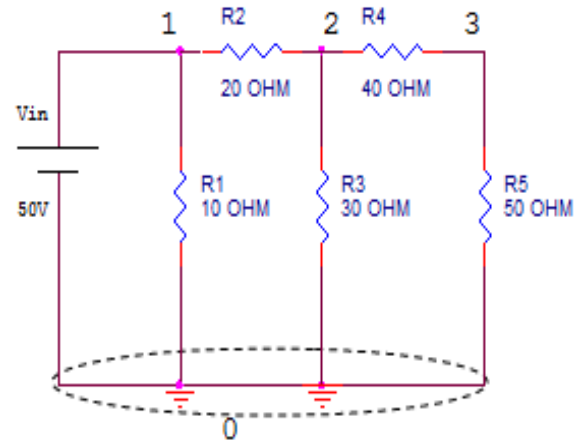Example #01:

Code:

```
Vs 1 0 50
R1 3 0 40
R2 2 3 20
R3 1 2 10
.DC Vs 0 50 50
.PRINT DC V(R1) V(R2) V(R3)
.PRINT DC I(R1) I(R2) I(R3)
.END
```



Output:

```
**** 03/27/21 09:22:36 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
```

Name: Ahmad Baseer Roll no:124

**** CIRCUIT DESCRIPTION

```
Vs 1 0 50
R1 3 0 40
R2 2 3 20
R3 1 2 10
.DC Vs 0 50 50
.PRINT DC V(R1) V(R2) V(R3)
.PRINT DC I(R1) I(R2) I(R3)
.END
```

```
**** 03/27/21 09:22:36 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
```

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

Vs	V(R1)	V(R2)	V(R3)
----	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00
5.000E+01	2.857E+01	1.429E+01	7.143E+00

```
**** 03/27/21 09:22:36 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
```

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

Vs	I(R1)	I(R2)	I(R3)
----	-------	-------	-------


0.000E+00	0.000E+00	0.000E+00	0.000E+00
5.000E+01	7.143E-01	7.143E-01	7.143E-01

Example #02:**Code:**

```

Vp 1 0 50
R1 1 0 10
R2 1 0 20
R3 1 0 40
.DC Vp 0 50 50
.PRINT DC V(R1) V(R2) V(R3)
.PRINT DC I(R1) I(R2) I(R3)
.END

```

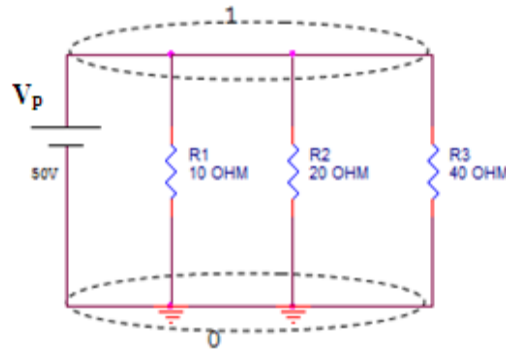**Output:**

```

**** 03/27/21 09:35:03 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer      Roll no:124
****   CIRCUIT DESCRIPTION
*****
Vp 1 0 50
R1 1 0 10
R2 1 0 20
R3 1 0 40
.DC Vp 0 50 50
.PRINT DC V(R1) V(R2) V(R3)
.PRINT DC I(R1) I(R2) I(R3)
.END
**** 03/27/21 09:35:03 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer      Roll no:124
****   DC TRANSFER CURVES      TEMPERATURE = 27.000 DEG C
*****

```

Vp	V(R1)	V(R2)	V(R3)
0.000E+00	0.000E+00	0.000E+00	0.000E+00
5.000E+01	5.000E+01	5.000E+01	5.000E+01

```

**** 03/27/21 09:35:03 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer      Roll no:124
****   DC TRANSFER CURVES      TEMPERATURE = 27.000 DEG C
*****

```


Vp	I(R1)	I(R2)	I(R3)
0.000E+00	0.000E+00	0.000E+00	0.000E+00
5.000E+01	5.000E+00	2.500E+00	1.250E+00

Example #03:**Code:**

```

Vin 1 0 50
R1 1 0 10
R2 1 2 20
R3 2 0 30
R4 2 3 40
R5 3 0 50
.DC Vin 0 50 50
.PRINT DC V(R1) V(R2) V(R3) V(R4) V(R5)
.PRINT DC I(R1) I(R2) I(R3) I(R4) I(R5)
.END

```

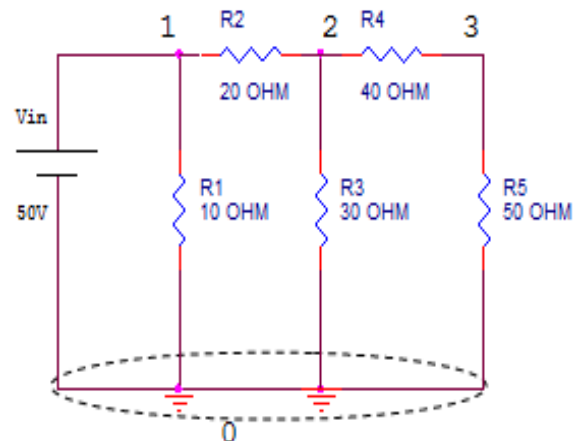

Output:

**** 03/27/21 09:44:25 ***** PSpice 9.2 (Mar 2000) ***** ID# 1 *****

Name: Ahmad Baseer Roll no:124

**** CIRCUIT DESCRIPTION

Vin 1 0 50

R1 1 0 10

R2 1 2 20

R3 2 0 30

R4 2 3 40

R5 3 0 50

.DC Vin 0 50 50

.PRINT DC V(R1) V(R2) V(R3) V(R4) V(R5)

.PRINT DC I(R1) I(R2) I(R3) I(R4) I(R5)

.END

**** 03/27/21 09:44:25 ***** PSpice 9.2 (Mar 2000) ***** ID# 1 *****

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

Vin	V(R1)	V(R2)	V(R3)	V(R4)	V(R5)
-----	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------

5.000E+01	5.000E+01	2.353E+01	2.647E+01	1.176E+01	1.471E+01
-----------	-----------	-----------	-----------	-----------	-----------

**** 03/27/21 09:44:25 ***** PSpice 9.2 (Mar 2000) ***** ID# 1 *****

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

Vin	I(R1)	I(R2)	I(R3)	I(R4)	I(R5)
-----	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------

5.000E+01	5.000E+00	1.176E+00	8.824E-01	2.941E-01	2.941E-01
-----------	-----------	-----------	-----------	-----------	-----------

Exercise #02: Write down the code in PSpice and find the voltage and current across each resistor and verify your result using manual calculations.

Code:

V 1 0 16.8

R1 1 2 124

R2 1 2 124

R3 2 3 4

R4 3 0 6

R5 3 0 3


R6 2 0 124

.DC V 0 16.8 16.8

.PRINT DC V(R1) V(R2) V(R3) V(R4) V(R5) V(R6)

.PRINT DC I(R1) I(R2) I(R3) I(R4) I(R5) I(R6)

.END

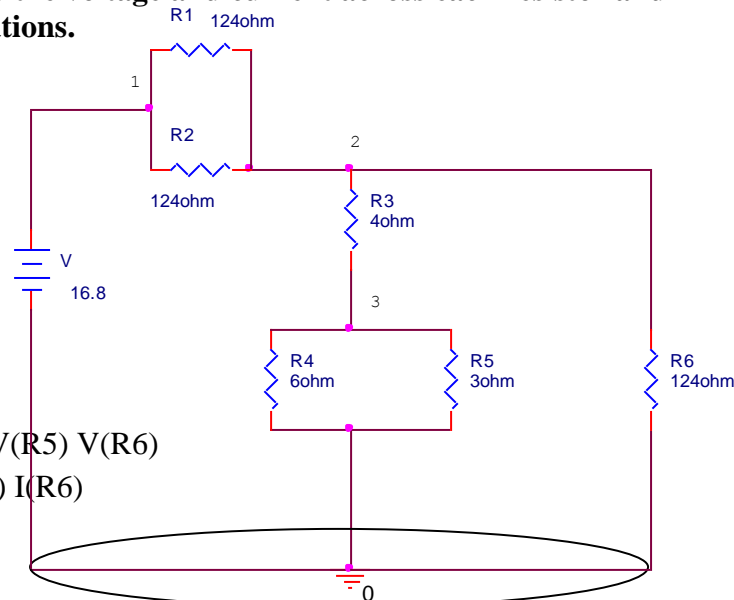

Ouput:

**** 03/27/21 10:30:17 ***** PSpice 9.2 (Mar 2000) ***** ID# 1 *****

Name: Ahmad Baseer Roll no:124

**** CIRCUIT DESCRIPTION

V 1 0 16.8

R1 1 2 124

R2 1 2 124

R3 2 3 4

R4 3 0 6

R5 3 0 3

R6 2 0 124

.DC V 0 16.8 16.8

.PRINT DC V(R1) V(R2) V(R3) V(R4) V(R5) V(R6)

.PRINT DC I(R1) I(R2) I(R3) I(R4) I(R5) I(R6)

.END

**** 03/27/21 10:30:17 ***** PSpice 9.2 (Mar 2000) ***** ID# 1 *****

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V	V(R1)	V(R2)	V(R3)	V(R4)	V(R5)	V(R6)
---	-------	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------	-----------

1.680E+01	1.538E+01	1.538E+01	9.465E-01	4.732E-01	4.732E-01	1.420E+00
-----------	-----------	-----------	-----------	-----------	-----------	-----------

**** 03/27/21 10:30:17 ***** PSpice 9.2 (Mar 2000) ***** ID# 1 *****

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V	I(R1)	I(R2)	I(R3)	I(R4)	I(R5)	I(R6)
---	-------	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------	-----------

1.680E+01	1.240E-01	1.240E-01	2.366E-01	7.887E-02	1.577E-01	1.145E-02
-----------	-----------	-----------	-----------	-----------	-----------	-----------

Exercise #03: Write down the code in PSpice and find the voltage and current across each component and verify your results using manual calculations.

Code:

V 1 0 10

R1 1 2 124

R2 2 3 124

R3 3 0 124

R4 3 0 124


R5 3 0 124

.DC V 0 10 10

.PRINT DC V(R1) V(R2) V(R3) V(R4) V(R5)

.PRINT DC I(R1) I(R2) I(R3) I(R4) I(R5)

.END

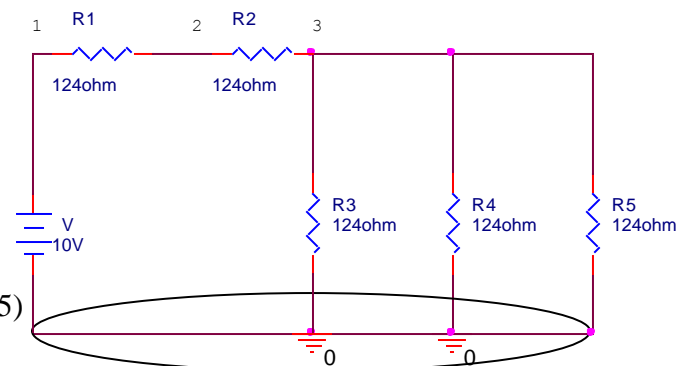

Output:

**** 03/27/21 10:58:16 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****

Name: Ahmad Baseer Roll no:124

**** CIRCUIT DESCRIPTION

V 1 0 10

R1 1 2 124

R2 2 3 124

R3 3 0 124

R4 3 0 124

R5 3 0 124

.DC V 0 10 10

.PRINT DC V(R1) V(R2) V(R3) V(R4) V(R5)

.PRINT DC I(R1) I(R2) I(R3) I(R4) I(R5)

.END

**** 03/27/21 10:58:16 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V	V(R1)	V(R2)	V(R3)	V(R4)	V(R5)
---	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------

1.000E+01	4.286E+00	4.286E+00	1.429E+00	1.429E+00	1.429E+00
-----------	-----------	-----------	-----------	-----------	-----------

**** 03/27/21 10:58:16 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****

Name: Ahmad Baseer Roll no:124

**** DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

V	I(R1)	I(R2)	I(R3)	I(R4)	I(R5)
---	-------	-------	-------	-------	-------

0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00	0.000E+00
-----------	-----------	-----------	-----------	-----------	-----------

1.000E+01	3.456E-02	3.456E-02	1.152E-02	1.152E-02	1.152E-02
-----------	-----------	-----------	-----------	-----------	-----------