


## LAB #0

**Objective:** Implementation of Simple RL Circuits and Finding Its Response.

**Exercise#01:** Apply the above code in PSpice and show the output and verify the result with manual calculation.

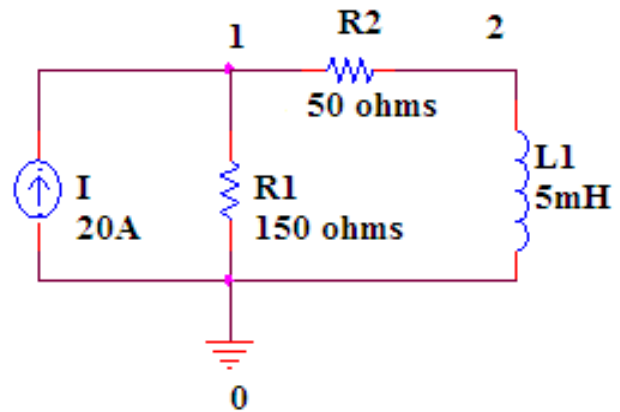**Example #01:**

```
I 1 0 20A
R1 1 0 150ohms
R2 1 2 50ohms
L1 2 0 5mH
.DC I 0 20 20
.PRINT DC V(R1) V(R2) V(L1)
.PRINT DC I(R1) I(R2) I(L1)
.options nopage
.END
```



**Output:**

\*\*\*\* 04/17/21 10:31:11 \*\*\*\*\* PSpice 9.2 (Mar 2000) \*\*\*\*\* ID# 1 \*\*\*\*\*

Name: Ahmad Baseer Roll no:124

\*\*\*\* CIRCUIT DESCRIPTION

\*\*\*\*\*

```
I 1 0 20A
R1 1 0 150ohms
R2 1 2 50ohms
L1 2 0 5mH
.DC I 0 20 20
.PRINT DC V(R1) V(R2) V(L1)
.PRINT DC I(R1) I(R2) I(L1)
.options nopage
.END
```

\*\*\*\* DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

| I | V(R1) | V(R2) | V(L1) |
|---|-------|-------|-------|
|---|-------|-------|-------|

|           |           |           |           |
|-----------|-----------|-----------|-----------|
| 0.000E+00 | 0.000E+00 | 0.000E+00 | 0.000E+00 |
|-----------|-----------|-----------|-----------|

|           |            |            |           |
|-----------|------------|------------|-----------|
| 2.000E+01 | -7.500E+02 | -7.500E+02 | 0.000E+00 |
|-----------|------------|------------|-----------|

\*\*\*\* DC TRANSFER CURVES TEMPERATURE = 27.000 DEG C

| I | I(R1) | I(R2) | I(L1) |
|---|-------|-------|-------|
|---|-------|-------|-------|

|           |           |           |           |
|-----------|-----------|-----------|-----------|
| 0.000E+00 | 0.000E+00 | 0.000E+00 | 0.000E+00 |
|-----------|-----------|-----------|-----------|


|           |            |            |            |
|-----------|------------|------------|------------|
| 2.000E+01 | -5.000E+00 | -1.500E+01 | -1.500E+01 |
|-----------|------------|------------|------------|

**Exercise#02: Write down the code in PSpice and find the voltage and current across each component (resistors and inductor).****Code:**

```

V1 1 0 100
R1 1 2 25ohms
L1 2 0 0.02H
R2 2 0 100ohms
.DC V1 0 100 100
.PRINT DC V(R1) V(R2) V(L1)
.PRINT DC I(R1) I(R2) I(L1)
.options nopage
.END

```

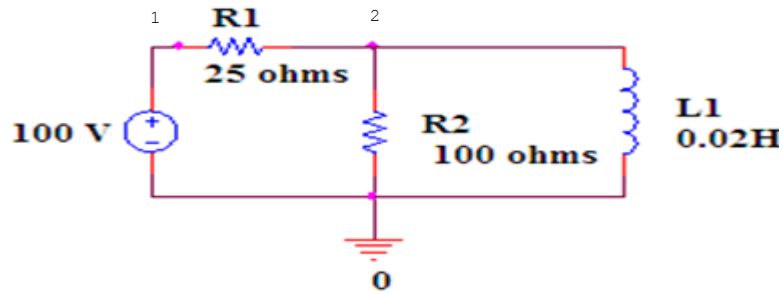**Output:**

```

**** 04/17/21 10:46:59 **** PSpice 9.2 (Mar 2000) **** ID# 1 ****
Name: Ahmad Baseer    Roll no:124
****  CIRCUIT DESCRIPTION
*****
V1 1 0 100
R1 1 2 25ohms
L1 2 0 0.02H
R2 2 0 100ohms
.DC V1 0 100 100
.PRINT DC V(R1) V(R2) V(L1)
.PRINT DC I(R1) I(R2) I(L1)
.options nopage
.END
****  DC TRANSFER CURVES          TEMPERATURE =  27.000 DEG C
V1          V(R1)      V(R2)      V(L1)

0.000E+00  0.000E+00  0.000E+00  0.000E+00
1.000E+02  1.000E+02  0.000E+00  0.000E+00
****  DC TRANSFER CURVES          TEMPERATURE =  27.000 DEG C
V1          I(R1)      I(R2)      I(L1)

0.000E+00  0.000E+00  0.000E+00  0.000E+00
1.000E+02  4.000E+00  0.000E+00  4.000E+00

```